

Printed Pages: 02

Paper Id:

1	8	0	4	0	1
---	---	---	---	---	---

Sub Code: EAG401/AG401

Roll No. XXXXXXXXXX

B. TECH.

**(SEM-IV) THEORY EXAMINATION 2017-18
ELECTRICAL CIRCUIT & MACHINE**

Time: 3 Hours**Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief. 2 x 10 = 20

- a. Explain the Kirchhoff's law.
- b. Explain low band pass filter.
- c. Dependent and independent sources.
- d. State and explain the maximum power transfer theorem.
- e. What do you mean by composite filters?
- f. Why carbon brushes are being used in d.c. machine?
- g. Under which situation during the measurement of 3 phase power by two wattmeter method, one wattmeter start giving reading in negative direction.
- h. RMS value of alternating current.
- i. Give the statement of Thevenin's theorem.
- j. What is meant by resonant frequency?

SECTION B


2. Attempt any three of the following: 10 x 3 = 30

- (a) What is armature reaction? Describe the effects of armature reaction on the operation of dc machines.
- (b) Why starter is required? Explain the construction and working of a three point starter.
- (c) The efficiency of a 1000 kVA, 110/220 V, 50 Hz, single phase transformer is 98.5% at half load and full load at 0.8 p.f. leading and 98.8% at full load unity p.f. Determine (i) Iron loss (ii) full load copper loss (iii) maximum efficiency at upf (iv) load kVA at maximum efficiency.
- (d) Discuss why single phase induction motors do not have starting torque. Explain its principle of operation and list various methods of starting.
Also discuss the speed-torque characteristic of any one of the 1phase induction motor.
- (e) Explain Thevenin's Norton superposition power transfer in detail.

SECTION C

3. Attempt any one part of the following: 10 x 1 = 10

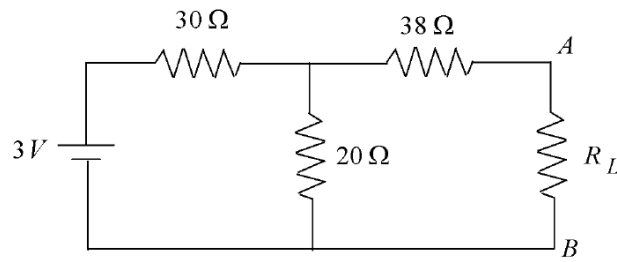- (a) Explain maximum power transfer theorem. Also find the value of load resistance R_L in the given diagram and determine the maximum power transferred.



- (b) Write short notes on
- (i) EMF and torque equation.
 - (ii) Leakage resistance
 - (iii) Voltage regulation
 - (iv) Hysteresis loss
4. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain the construction and working of poly phase induction motor with circuit and phasor diagram.
 - (b) Why starter are necessary for starting of 3 phase induction motor? Explain the working of rotor resistance starter for 3 phase slip ring induction motor.
5. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain the terms average power, power factor, Instantaneous power and reactive power.
 - (b) Explain the procedure to convert star connected network into delta connected network and delta connected network into star connected network.
6. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain the speed control methods of DC Motor.
 - (b) Why improvement of power factor is needed? Explain.
7. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain two wattmeter method of measurement of 3 phase power with the help of circuit and phasor diagram.
 - (b) A voltage waveform is given by expression $v = 150 \sin(520t + 50)$. Determine :
 - (i) Maximum Value
 - (ii) RMS Value
 - (iii) Frequency
 - (iv) Time Period
 - (v) Phase angle of voltage