

**B. TECH**  
**(SEM. IV) THEORY EXAMINATION 2017-18**  
**ELECTRONIC MEASUREMENTS AND INSTRUMENTATION**

Time: 3 Hours

Total Marks: 100

- Note:** 1. Attempt all Sections.  
2. Assume any missing data.

**SECTION A**

1. Attempt *all* questions in brief. **2 x 10 = 20**
- Determine the dimensions of force, work, energy and power.
  - Define accuracy and precision with suitable example.
  - What is the principle of ramp type digital voltmeter?
  - Explain rise time and fall time with neat diagram.
  - Name the bridge circuits used for the measurement of self inductance.
  - What are the criteria for balance of a Wheatstone bridge?
  - Why triggering is needed in CRO?
  - List the main parts of CRT.
  - What are the advantages of digital instruments over analog instruments?
  - What are the different calibration methodologies?

**SECTION B**

2. Attempt any *three* of the following: **10 x 3 = 30**
- Explain different types of errors that may occur in measurements. Differentiate between gross errors and systematic errors. List a few ways of minimizing the effect of errors in measurement.
  - Explain multimeter probes. What are the two methods of measuring current using high current probes of multimeter?
  - Define the Q-factor of a coil. Explain with a circuit diagram the construction and principle of operation of a basic Q-meter?
  - Draw the basic block diagram of an oscilloscope and state the function of each block.
  - On what factors does the frequency of instrumentation calibration depend? Explain how A.C. voltmeter calibration can be done.

**SECTION C**

3. Attempt any *one* parts of the following: **10 x 1 = 10**
- Describe the principle of operation, advantages, disadvantages and application of PMMC.
  - Describe the principle of operation and use of Galvanometer in detail with suitable diagram.
4. Attempt any *one* parts of the following: **10 x 1 = 10**
- Draw and explain the block diagram of the Ramp Type DVM with its system waveform. Compare digital and analog Multimeter.
  - Draw and explain the block diagram of a digital frequency meter system in detail.

**5. Attempt any one parts of the following:**

**10 x 1 = 10**

- a) State various methods of measurement of low resistance. Why ammeter-voltmeter methods not suitable for the precise measurement of low resistance?
- b) Derive an expression for finding unknown resistance and Inductance for Maxwell Bridge.

**6. Attempt any one parts of the following:**

**10 x 1 = 10**

- a) Describe with block diagram the operation of a digital storage CRO (DSO). State the function of each block. Also write its applications.
- b) Explain CRO probe and Sampling Oscilloscope in detail with suitable diagram.

**7. Attempt any one parts of the following:**

**10 x 1 = 10**

- a) Describe with the help of a block diagram the operation of a X-Y recorder. Also list the application of X-Y recorder.
- b) Draw and explain the circuits for calibration of d.c. voltmeter and wattmeter with standard instruments.