

(Following Paper ID and Roll No. to be filled in your
Answer Books)

Paper ID : 131403

Roll No.

--	--	--	--	--	--	--	--	--	--

B. TECH.

Theory Examination (Semester-IV) 2015-16

**ELECTRONIC MEASUREMENT AND
INSTRUMENTATION**

Time : 3 Hours

Max. Marks : 100

Note: Attempt questions from all sections as per instructions.

Section-A

- 1. Attempt all questions. All questions carry equal marks.**
(2×10=20)

- (a) What do you mean by high current prob?
- (b) Calculate the maximum percentage error in the difference of two measured voltage when $v_1 = 100 \pm 1\%$ and $v_2 = 80 \pm 5\%$.
- (c) What do you mean by engineering notation?

- (d) Three resistances have the following rating $R_1=15\Omega \pm 5\%$, $R_2=33\Omega \pm 2\%$, $R_3=75\Omega \pm 5\%$. Determine the magnitude and limiting error in ohms if resistance is connected in series.
- (e) What are 1:1 & 10:1 probes in oscilloscopes?
- (f) What is mean by interpolation in oscilloscope system?
- (g) What is mean by voltage sensitivity in measuring instrument?
- (h) Define the systematic error, observational error with example.
- (i) Define swamping resistance used in PMMC instrument.
- (f) Define the term resolution.

Section-B

2. Attempt any five questions. All questions carry equal marks. (10×5=50)

- (a) The bridge is balanced at 1000 Hz. It has following components
- (i) Arm ab = 0.2micro farad capacitance

- (ii) Arm bc = a pure resistor of 500 ohms.
- (iii) Arm da- 300 ohms resistor R in parallel with unknown capacitor $C=0.1$ micro farad.
- (iv) Find the constants of Arm cd- considering it as series circuit.
- (b) What is voltmeter and ammeter method for measuring the resistance? Draw suitable diagram.
- (c) Derive the balancing equation for Kelvin double bridge with proper circuit diagram.
- (d) Explain the XY recorder with the help of Block diagram.
- (e) Explain the Digital frequency meter system for forward counting using suitable diagram.
- (f) The ten reading noted when measuring current are : 41.7, 42.0, 41.8, 42.0, 42.1, 41.9, 42.0, 41.9, 42.5, & 41.8 amp Find (i) Mean (ii) Standard Deviation (iii) Probable error of one reading (iv) Probable error of the mean (v) range
- (g) Explain the difference amplifier voltmeter system with proper circuit diagram.

(h) Explain the following measurement standard :

(i) International standard

(ii) Secondary standard

(iii) Primary standard

(iv) Working standard

Section-C

Attempt any two questions. All questions carry equal marks.

(15×2=30)

3. Draw and explain the different type of oscilloscopes .
4. Derive the equation for maxwell bridge and solve a maxwell inductance bridge using a standard capacitor $C_3 = 0.1$ micro farad and operate at a supply frequency of 100Hz. Balance is achieved when $R_1 = 1.26$ kohms, $R_3 = 470$ Ohms, and $R_4 = 500$ Ohms. Calculate the inductance and resistance of the measured inductor, and determine its Q factor.
5. Write short note on following :-
 - (i) Strip chart recorders
 - (ii) PMMC Instrument