

(Following Paper ID and Roll No. to be filled in your
Answer Books)

Paper ID : 160407

Roll No.

--	--	--	--	--	--	--	--	--	--

B.TECH.


Theory Examination (Semester-IV) 2015-16

NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours

Max. Marks : 100

Note : Attempt all questions

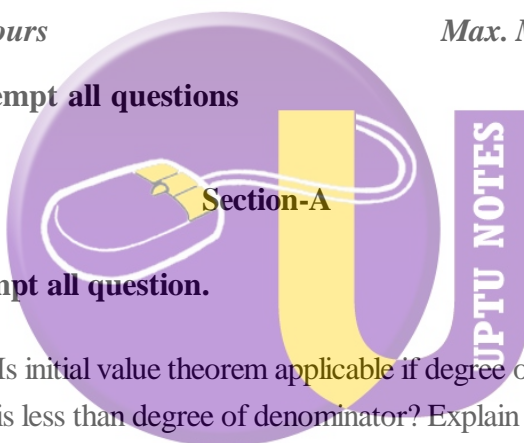

1. Attempt all question. (2×10=20)


- (a) Is initial value theorem applicable if degree of numerators is less than degree of denominator? Explain with any one example.
- (b) Define link, Twigs and Datum node in Graph Theory.
- (c) Write properties of L C Admittance functions.
- (d) Write properties of positive real function.
- (e) Explain incidence matrix with example.

- (f) Define open circuit parameters.
- (g) What do you mean by Transfer impedance?
- (h) Write the statement of Millman theorem using complex load.
- (i) What is the condition to transfer maximum power?
- (j) Check whether the given polynomial $P(s) = s^4 + s^3 + 2s^2 + 4s + 1$ is Hurwitz or not.


Section-B

2. Attempt any five parts of the following question. [10×5=50]

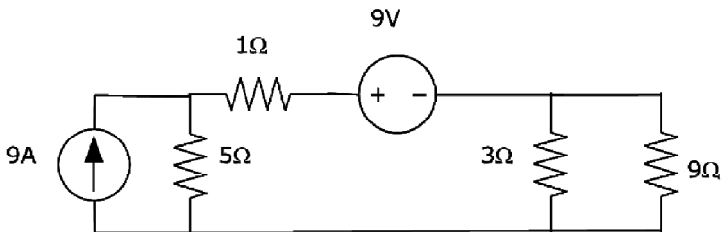
- (a) State and explain superposition theorem. Find the current in 3Ω resistance using superposition theorem for the circuit shown in Fig.



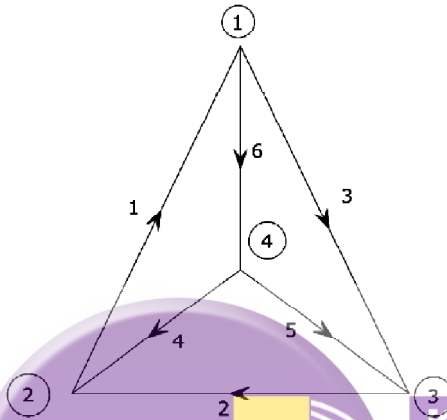- (b) What do you mean by oriented graph, evaluate incidence matrix & cut set matrix of the graph given in fig Below.




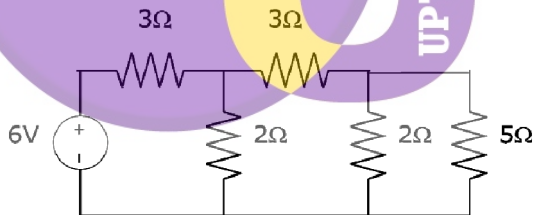- (c) Write the statement of Norton theorem. Find the current in 5Ω resistor by using this theorem as shown in fig.



- (d) Derive the Max Power Transfer theorem, & prove that for max power transfer internal resistance equal to load resistance.

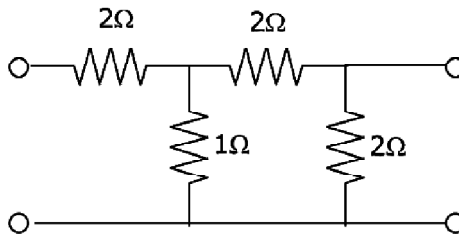- (e) Determine the Z parameters of circuit shown in figure .




- (f) (i) Explain different type of network parameters like z, h, y etc.
- (ii) Write the properties of transfer function.
- (g) Explain the properties of Hurwitz polynomial & check whether polynomial Hurwitz or not? $P(s) = s^4 + s^3 + 2s^2 + 3s + 2$
- (h) Determine whether the function $Z(s) = 2s^2 + 5/s(s^2 + 1)$ is positive real or not. Also write the property of positive real function.

Section-C

Attempt any two of following questions.

(15×2=30)

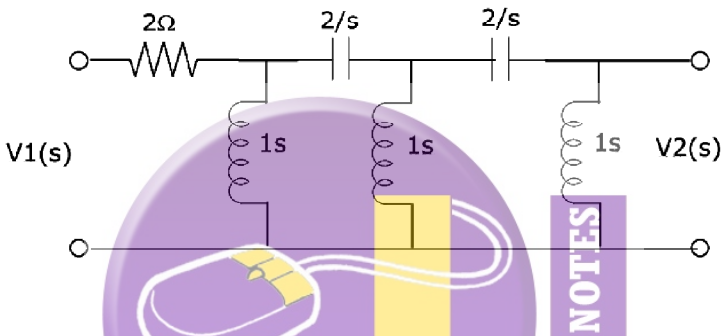3. Determine the voltage transfer function $V_2(s) / V_1(s)$ for the network shown in figure below :



4. (i) Using the Foster (I), synthesize the function

$$Y(s) = \frac{(s^2+5)(s^2+13)}{s(s^2+9)}$$

- (ii) Diagnose whether the following impedance function represents a RL or RC network and find its first cauer form

$$Z(s) = \frac{(s+4)(s+6)}{(s+3)(s+5)}$$

5. Define the following :

(i) Cut-set matrix

(ii) branch

(iii) tree

(iv) incidence matrix

